

HW #5

Calculate and plot the frequency response, impulse response, and the step response for second order RC the system shown.

Deadline is Monday 27th March.

